

EEL2020 Digital Design Lab Report

Sem II AY 2023-24

Experiment No.	:	08
Name	:	Lavangi Parihar
Roll No.	:	B22EE044
Partner Name (Roll Number)	:	Mansi Choudhary (B22EE045)


Objective

To implement a 4-bit serial adder using Verilog on the PYNQ Z2 Development Board using the Vivado Design Suite

Logic Design

A Serial adder performs bit by bit addition. Two shift registers are used to store the binary numbers that are to be added.

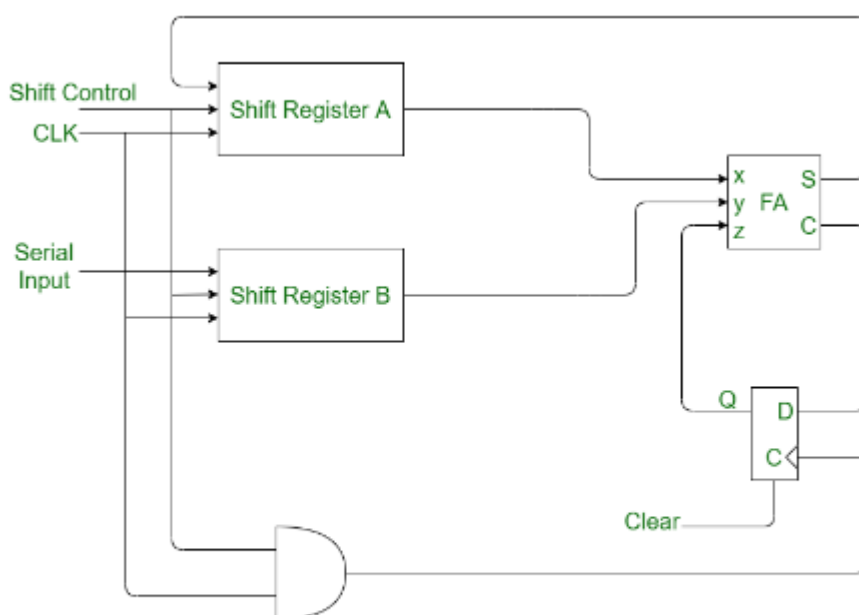A single full adder is used to add one pair of bits at a time along with the carry. The carry output from the full adder is applied to a D flip flop. After that output is used as carry for next significant bits. The sum bit from the output of the full adder can be transferred into a third shift register.



Block Diagram of Serial Binary Adder

Source Description

- Design source

```
module serialadder(DATA, loadA, loadB, start, clk, regA, regB, rst, co, cout_f);
input [3:0] DATA;
input loadA, loadB, start, clk, rst;
output reg [3:0] regA, regB;
output co;
output reg cout_f;

reg cin;
reg [27:0] count=0;
wire w1, w2, w3, cout, sum;

// CLK DIV
assign co = count[27];
always@(posedge clk)
count = count + 1;

// 1 bit FA
xor(sum, regA[0], regB[0], cin);
and(w1, regA[0], regB[0]);
and(w2, regA[0], cin);
and(w3, regB[0], cin);
or(cout, w1, w2, w3);

always@(posedge co)
begin
if (rst)
begin
regA <= 4'b0000;
regB <= 4'b0000;
cin <= 1'b0;
end
else if(loadA)
regA <= DATA;
else if(loadB)
```

```

    regB <= DATA;
else if (start)
    begin
        regB <= regB >> 1;
        regA <= regA >> 1;
        regA[3] <= sum;
        cin <= cout;
        cout_f <= cout;
    end
end

endmodule

```

- [Constraint file](#)

The XDC file was updated with the following changes:

Ports (from Verilog module)	PYNQ Component Type
clk	H16
start	M20
rst	M19
co	N15
regA	R14 P14 N16 M14
DATA	D19 D20 L20 L19

The RPI file was updated with the following changes:

Ports (from Verilog module)	PRI Component Type
regB	B20 W8 U8 W6
cout_f	F20
loadA	V6
loadB	Y6

- [Simulation source](#) (if any)

```
module tb_example();
// Inputs
reg clk, rst, loadA, loadB, start;
reg [3:0] DATA;

// Outputs
wire [3:0] regA, regB;
wire co,cout_f;

// Instantiate the design module
serialadder dut (
    .clk(clk),
    .rst(rst),
    .loadA(loadA),
    .loadB(loadB),
    .start(start),
    .regA(regA),
    .regB(regB),
    .DATA(DATA),
    .co(co),
    .cout_f(cout_f)
);

// Clock generation
always #5 clk = ~clk;
// Test stimulus
initial begin
    // Initialize inputs
    clk = 0;
    rst = 1;
    loadA = 0;
    loadB = 0;
    start = 0;
    DATA = 4'b1010; // Example input

// Apply reset
    #10;
    rst=0;
```

```
// Load data into register A
loadA = 1;
DATA = 4'b1100; // New example input for register A
#10;
loadA = 0;
```

```
// Load data into register B
loadB = 1;
DATA = 4'b0110; // New example input for register B
#10;
loadB = 0;
```

```
// Start the process
start = 1;
#40;
start = 0;
#10;
rst=1;
#10;
```

```
rst=1;
DATA=4'b0010;
#10;
```


```
rst=0;
loadA=1;
#10;
loadA=0;
#10;
DATA=4'b0101;
loadB=1;
#20;
loadB=0;
start=1;
#40;
start=0;
#20
```

```
// End simulation
$finish;
```


end

endmodule

Simulation Results (Timing diagram)

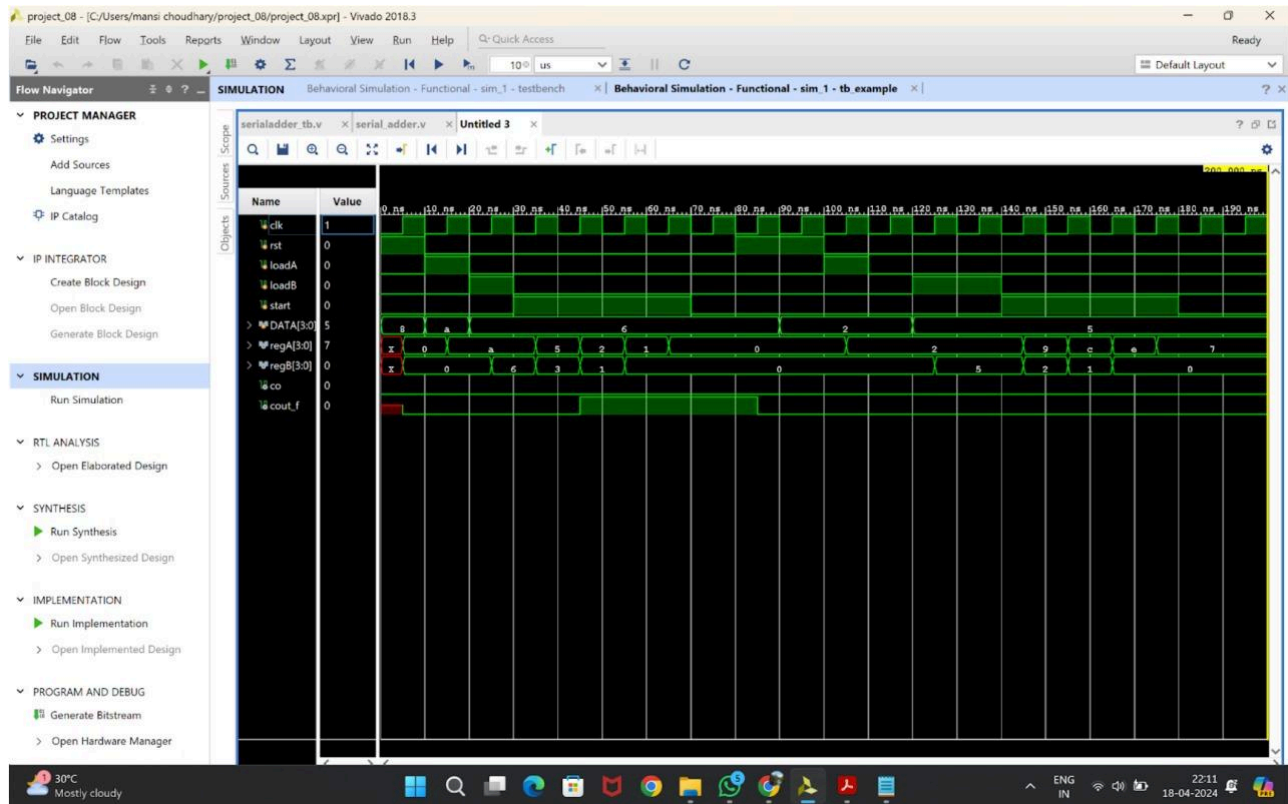

Elaborated Design

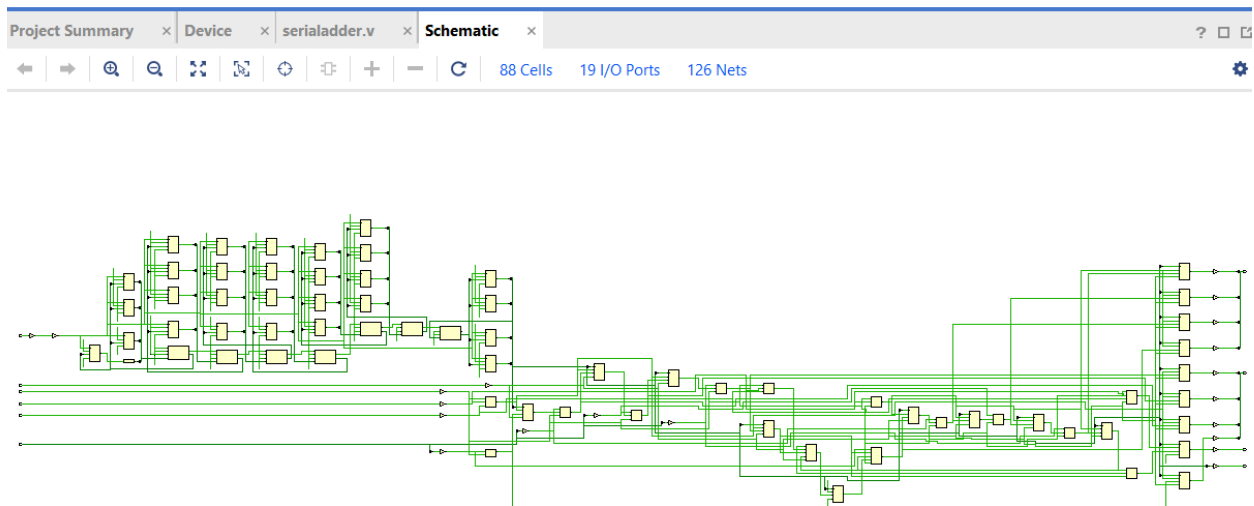

PYNQ Working Video
[Video Link](#)